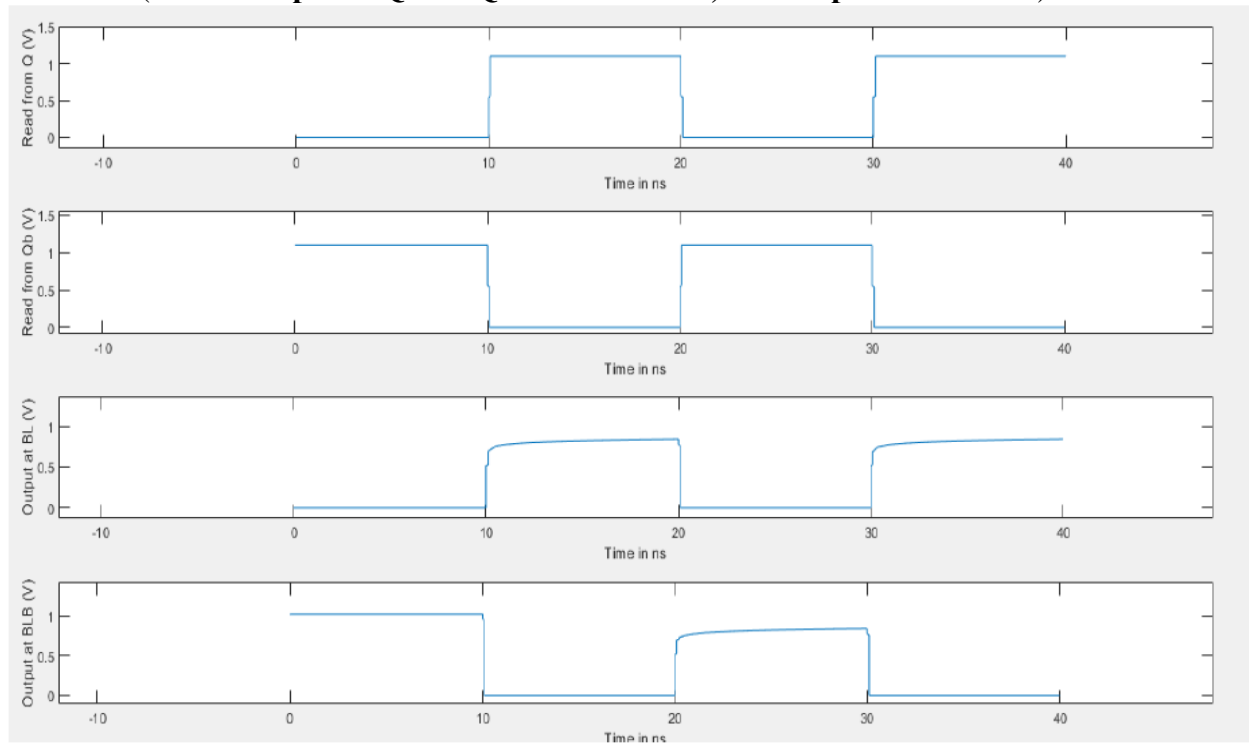


Read Plot (To read input at Q and Qb WL is set to 1, and output is seen at B)



Write Plot (To write a bit WL is set to 1, BL is set to the input value and the value of BL is stored at Q)

